

Sequential Circuits Cheat Sheet (Theory Only)

1. Introduction to Sequential Circuits

Sequential Circuits → Digital circuits where output depends on **both present inputs and past states** (memory is involved).

Two main components:

- **Combinational Logic (Logic Gates).**
- **Storage Elements (Latches, Flip-Flops).**

Types of Sequential Circuits:

- **Synchronous** → Clock-controlled.
 - **Asynchronous** → Output changes immediately with input.
-

2. Latches

Latches are basic memory elements that store **1-bit data**.

They are **level-triggered** (change state based on input).

(A) SR Latch (Set-Reset Latch)

Inputs: S (Set) and R (Reset).

Outputs: Q and Q' (complement of Q).

Operation:

- S = 1, R = 0 → Q = 1 (Set).
- S = 0, R = 1 → Q = 0 (Reset).
- S = 0, R = 0 → No change (Previous State).
- S = 1, R = 1 → **Invalid State**.

SR Latch Truth Table:

S	R	Q (Next State)	Q'
0	0	No Change	-
0	1	0 (Reset)	1
1	0	1 (Set)	0
1	1	Invalid	-

(B) D Latch (Data Latch)

Eliminates the invalid state of the SR latch.

Single input (D) and Clock (C).

Operation:

- D = 1 → Q = 1 (Set).
- D = 0 → Q = 0 (Reset).

Truth Table:

D	Clock	Q (Next State)	---	-----	-----	0	1	0 (Reset)	1	1	1 (Set)	X	0	No Change
---	-------	----------------	-----	-------	-------	---	---	-----------	---	---	---------	---	---	-----------

3. Flip-Flops

Flip-Flops are **edge-triggered storage elements** (change state only on the clock edge).

Types of Flip-Flops:

(A) RS Flip-Flop (Edge-Triggered SR Latch)

Works like SR Latch but with a clock signal.

Truth Table:

S	R	Q (Next State)
0	0	No Change
0	1	0 (Reset)
1	0	1 (Set)
1	1	Invalid

(B) JK Flip-Flop

Improves RS Flip-Flop (No invalid state).

Truth Table:

J	K	Q (Next State)
0	0	No Change
0	1	0 (Reset)
1	0	1 (Set)
1	1	Toggle

Toggle condition (J=1, K=1) changes state every clock cycle.

(C) D Flip-Flop (Data Flip-Flop)

Stores one-bit data (Prevents glitches).

Truth Table:

D	Clock	Q (Next State)
0	↑	0 (Reset)
1	↑	1 (Set)

(D) T Flip-Flop (Toggle Flip-Flop)

Toggles (Flips) output every clock pulse.

Truth Table:

T	Clock	Q (Next State)
0	↑	No Change
1	↑	Toggle

Used in Counters.

4. Excitation Table of Flip-Flops

Used to design sequential circuits (reverse engineering truth tables).

Flip-Flop	Current State (Q)	Next State (Q_{n+1})	Input Needed
RS	$0 \rightarrow 0$	No Change	S=0, R=0
RS	$0 \rightarrow 1$	Set	S=1, R=0

Flip-Flop	Current State (Q)	Next State (Q_{n+1})	Input Needed
RS	$1 \rightarrow 0$	Reset	$S=0, R=1$
JK	$0 \rightarrow 1$	Set	$J=1, K=0$
JK	$1 \rightarrow 0$	Reset	$J=0, K=1$
JK	Toggle	Toggle	$J=1, K=1$
D	$0 \rightarrow 1$	Load 1	$D=1$
T	Toggle	Flip State	$T=1$

5. Counters

Counters store and count values on clock pulses.
Types:

(A) Asynchronous Counters (Ripple Counters)

Each Flip-Flop toggles the next one.
Slower due to propagation delay.

(B) Synchronous Counters

All Flip-Flops change at the same time (faster).

(C) MOD Counters

Counts up to n states (MOD-n counter).
Example: MOD-4 counter counts $0 \rightarrow 1 \rightarrow 2 \rightarrow 3 \rightarrow 0$.

(D) Johnson Counter

Modified ring counter with feedback.
Generates $2n$ unique states using n Flip-Flops.

6. Shift Registers

Stores and shifts data in bit sequences.
Types of Shift Registers:

Type	Function
SISO (Serial In Serial Out)	Shifts data one bit at a time
SIPO (Serial In Parallel Out)	Serial input, Parallel readout
PISO (Parallel In Serial Out)	Parallel input, Serial readout
PIPO (Parallel In Parallel Out)	Parallel input & Parallel output
Universal Shift Register	Can perform all operations (SISO, SIPO, PISO, PIPO)

7. Ripple Counter

A type of Asynchronous Counter where the flip-flop output acts as the clock for the next flip-flop.
Example: 4-bit Ripple Counter (counts 0000 to 1111).

Comparison of Sequential Circuits

Feature	Latches	Flip-Flops	Counters	Shift Registers
Triggering	Level	Edge	Edge	Edge
Storage	1-bit	1-bit	Multiple bits	Multiple bits
Uses	Simple memory	Storage & Timing	Counting & Frequency Division	Data Transfer

Key Takeaways

- Sequential Circuits have memory (store past states).
 - Latches (SR, D) store bits based on input levels.
 - Flip-Flops (RS, JK, D, T) are edge-triggered storage devices.
 - Counters (Async/Sync, MOD, Johnson) are used for counting events.
 - Shift Registers shift bits in multiple configurations.
-

This Sequential Circuits Cheat Sheet covers latches, flip-flops, excitation tables, counters, and shift registers.
Let me know if you need further explanations!