

## Bipolar Junction Transistor (BJT)

### Construction & Operation

- **BJT:** A three-layer semiconductor device with **Emitter (E)**, **Base (B)**, and **Collector (C)**.
- **Types:**
  - **NPN:** Current flows from collector to emitter.
  - **PNP:** Current flows from emitter to collector.
  -
- **Operation:** Works by controlling a small base current to regulate a larger collector current.

### BJT Configurations & Characteristics

#### 1st Common Base (CB):

- Low input impedance, high output impedance.
- Voltage gain is high, but current gain is less than 1.
- 

#### 2nd Common Emitter (CE):

- Most used configuration.
- High voltage and current gain.
- Provides phase inversion.
- 

#### 3rd Common Collector (CC):

- Also called an **emitter follower**.
- High input impedance, low output impedance.
- Voltage gain  $\approx 1$ , but high current gain.
- 

### Biassing of BJT

- Ensures **stable operation** of the transistor in amplification mode.
  - Types of Biassing:
    - **Fixed Bias**
    - **Collector-to-Base Bias**
    - **Voltage Divider Bias** (most stable method).
    -
- 

## Junction Field Effect Transistor (JFET)

### Construction & Operation

- **JFET:** A unipolar device controlled by voltage, with terminals **Drain (D)**, **Source (S)**, and **Gate (G)**.
  - **Types:**
    - **N-channel JFET:** Majority carriers are electrons.
    - **P-channel JFET:** Majority carriers are holes.
    -
  - **Operation:**
    - When voltage at the **Gate** is negative (for N-channel), the conduction channel narrows, reducing current.
    - No gate current flows, making it **highly efficient**.
    -
- 

## Metal Oxide Semiconductor Field Effect Transistor (MOSFET)

## Types of MOSFET

### 1st Enhancement MOSFET (EMOSFET)

- 
- No conduction at zero gate voltage.
- Needs a **positive voltage** (N-channel) or **negative voltage** (P-channel) to conduct.
- 

### 2nd Depletion MOSFET (DMOSFET)

- 
- Conducts even at zero gate voltage.
- Can operate in both enhancement and depletion modes.
- 

## MOSFET Operation Characteristics

- High input impedance (ideal for signal amplification).
- Faster switching speed than BJTs (used in digital circuits).
- Less power consumption, making it suitable for low-power applications.