

Sequential Logic Design

Author : AI Generated

Date : 2025-01-30

Sequential Circuits and Counters

Introduction to Sequential Circuits:

- Circuits with memory, output depends on past and present inputs.

Latches and Flip-Flops:

- **SR Latch and D Latch:** Basic memory elements.
- **Flip-Flops (FFs):** RS, JK, D, and T Flip-Flops.
- **Excitation Table of Flip-Flops:** Determines the required inputs for state transitions.

Counters:

- **Asynchronous Counters (Ripple Counter):** Clock input applied to first FF, others toggle asynchronously.
- **Synchronous Counters:** All FFs triggered simultaneously.
- **Mod Counters:** Counters with a modulus value.

Shift Registers:

- Used for data storage and transfer.
- Types: **SISO (Serial In Serial Out)**, **SIPO (Serial In Parallel Out)**, **PISO (Parallel In Serial Out)**, **PIPO (Parallel In Parallel Out)**, and **Universal Shift Registers**.

Special Counters:

- **Ripple Counter:** Counts asynchronously.
- **Johnson Counter:** Circular shift register with feedback.

